

Circuit Simulation Lab: 4

Encoders

Introduction


The purpose of this experiment is to introduce the design of simple combinational circuits, in this case Encoders. An Encoder is a combinational circuit that performs the reverse operation of Decoder. It has maximum of 2^n input lines and 'n' output lines. It will produce a binary code equivalent to the input, which is active High. Therefore, the encoder encodes 2^n input lines with 'n' bits. It is optional to represent the enable signal in encoders.

Software tools Requirement

Modelsim (Siemens)


Xilinx Vivado

Logic Diagram

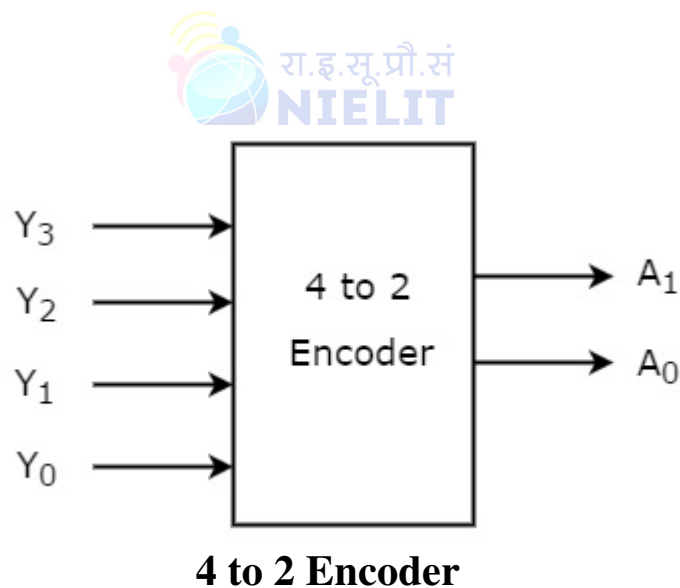

Inputs				Outputs	
Y_3	Y_2	Y_1	Y_0	A_1	A_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

Truth Table

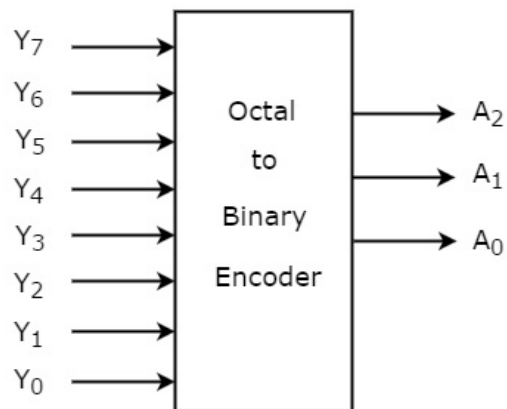

Octal to Binary Encoder

Describe the above circuits in Verilog HDL and capture the Waveforms

- 1. Dataflow modeling*
- 2. Behavior modeling*
- 3. Structural modeling*

Questions to answered after this lab

- 1. Implement full adder by using suitable decoder.*
- 2. Write short notes on “test bench” with examples.*