

Circuit Simulation Lab:23

Design of Counters

Introduction


The purpose of this experiment is to introduce the design of Ring Counter.

A ring counter is a type of counter composed of flip-flops connected into a shift register, with the output of the last flip-flop fed to the input of the first, making a "circular" or "ring" structure.

Software tools Requirement

Modelsim (Siemens)

Xilinx Vivado

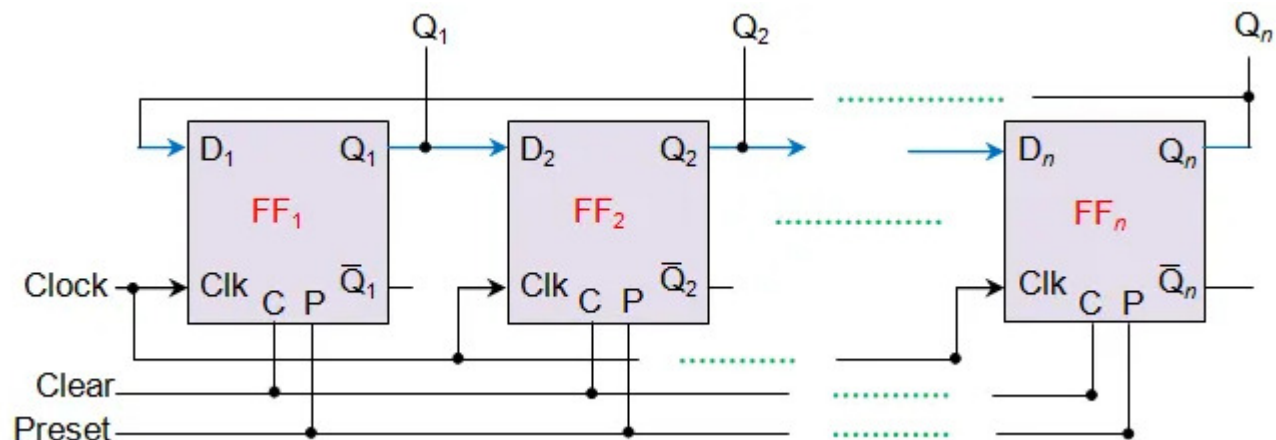

n bit Ring Counter

Expected Waveform



Design the above behavior in Verilog HDL and write its testbench and capture the Waveforms

Use Behavior modeling or Structural Modeling

