

Circuit Simulation Lab:24

Design of Counters

Introduction


The purpose of this experiment is to introduce the design of Johnson Counter.

In Johnson counter, the complemented output of last flip flop is connected to input of first flip flop and to implement n-bit Johnson counter we require n flip-flop

Software tools Requirement

Modelsim (Siemens)

Xilinx Vivado

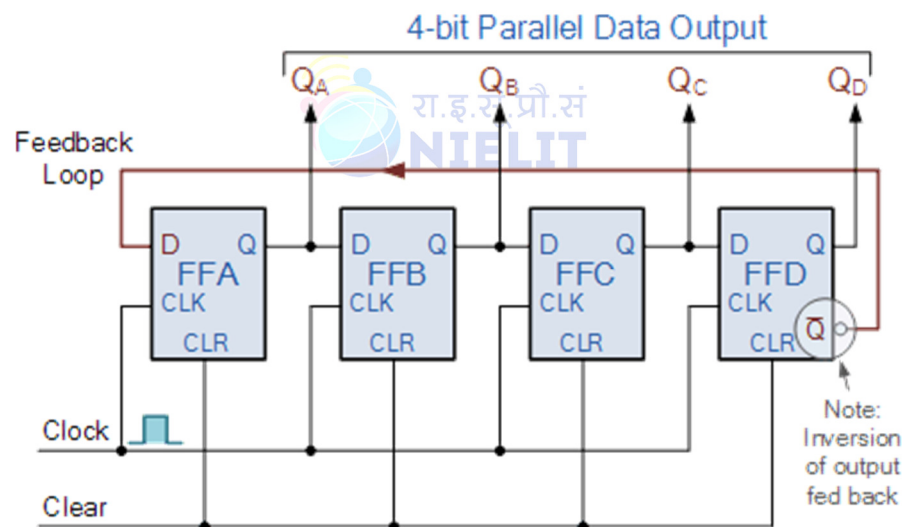

4 bit Johnson Counter

Design the above behavior in Verilog HDL and write its testbench and capture the Waveforms,

Use Behavior modeling or Structural Modeling