

Introduction to AXI-Lite	2
1. Title.....	2
2. Objective	2
3. Theory (Multi-Level)	2
3.1 Beginner — Simple Intuition	2
3.2 Intermediate — Engineering View	3
3.3 Advanced — Signal/Architecture Level.....	3
4. Architecture / Concept.....	4
Standalone AXI-Lite Educational Model	4
AXI-Lite Slave State Machines (from tb_axi_lite_standalone.v)	4
5. Implementation	5
Files in This Module	5
Standalone Testbench Key Tasks (tb_axi_lite_standalone.v)	5
Slave Register Map (axi_lite_slave in standalone TB)	5
6. Lab / Hands-on Section.....	6
Step 1: Run the Standalone AXI-Lite Testbench.....	6
Expected Terminal Output.....	6
Step 2: View Waveforms.....	7
Step 3: Run Full AXI-UART Testbench	7
7. Waveform / Verification Insight.....	8
Write Transaction in GTKWave	8
Read Transaction in GTKWave.....	8
Timing Measurement.....	8
8. Common Issues & Debug Tips.....	9
AXI Protocol Violation Checklist.....	9
9. Summary	9

Introduction to AXI-Lite

Course: PicoRV32 SoC Subsystem with AXI-Lite & UART Integration

1. Title

Introduction to AXI-Lite — Valid/Ready Handshake and Channel Architecture

2. Objective

By the end of this module, learners will be able to:

- Describe the five AXI-Lite channel types and their direction
- Explain the valid/ready handshake mechanism and its rules
- Trace a complete write transaction ($AW \rightarrow W \rightarrow B$) through waveforms
- Trace a complete read transaction ($AR \rightarrow R$) through waveforms
- Run the standalone AXI-Lite testbench (`tb_axi_lite_standalone.v`) and verify the handshake

3. Theory (Multi-Level)

3.1 Beginner — Simple Intuition

Imagine AXI-Lite as a two-person handshake:

- The **master** (e.g., a CPU) says “I have something for you” by raising **VALID**
- The **slave** (e.g., a peripheral) says “I’m ready to receive” by raising **READY**
- The actual transfer (handshake) only happens **when BOTH are high at the same clock edge**

This means the master and slave can independently assert their signals without knowing each other’s timing — a protocol designed for modular, decoupled hardware blocks.

Write operation analogy (posting a letter):

1. You (master) write the address on the envelope → **AW channel**
2. You put the letter in the envelope (data) → **W channel**
3. The post office confirms delivery → **B channel (response)**

Read operation analogy (fetching a file):

1. You request a file by name → **AR channel**
2. The librarian hands you the file → **R channel**

3.2 Intermediate — Engineering View


AXI4-Lite is a simplified subset of ARM's AMBA AXI4 protocol, designed for register-level peripheral access. It has:

Channel	Direction	Signals
Write Address (AW)	Master → Slave	AWADDR[31:0], AWVALID, AWREADY
Write Data (W)	Master → Slave	WDATA[31:0],WSTRB[3:0], WVALID, WREADY
Write Response (B)	Slave → Master	BRESP[1:0], BVALID, BREADY
Read Address (AR)	Master → Slave	ARADDR[31:0], ARVALID, ARREADY
Read Data (R)	Slave → Master	RDATA[31:0], RRESP[1:0], RVALID, RREADY

Handshake Golden Rule: > A transaction occurs at the rising clock edge when **VALID AND READY** are both 1.

Key constraints: - Master can assert VALID without knowing if slave is ready - Slave can assert READY without VALID being high (pre-ready) - Master **MUST NOT** de-assert VALID before a handshake completes - BRESP/RRESP = 2'b00 means OKAY (no error) -WSTRB is a **byte-enable**: bit 0 controls bytes [7:0], bit 1 → [15:8], etc.

3.3 Advanced — Signal/Architecture Level

 

Why separate AW and W channels? This decoupling allows a slave to accept an address before it is ready to accept data, and vice versa — enabling pipelining and burst (in AXI4 full) optimization.


WSTRB encoding:

WSTRB = 4'hF → Write all 4 bytes (common case, 32-bit register write)
WSTRB = 4'h1 → Write byte [7:0] only
WSTRB = 4'h3 → Write bytes [15:0] only
WSTRB = 4'h0 → No write (bypass)

 4. Architecture / Concept

Standalone AXI-Lite Educational Model

The testbench `tb/tb_axi_lite_standalone.v` implements a complete self-contained demonstration:



AXI-Lite Slave State Machines (from `tb_axi_lite_standalone.v`)

Write FSM:

IDLE → (awvalid asserted) → WR_ADDR (latch addr)
WR_ADDR → (wvalid asserted) → WR_DATA (latch data, write to reg)

WR_DATA → (always) → WR_RESP (assert bvalid)

WR_RESP → (bvalid & bready) → IDLE

Read FSM:

IDLE → (arvalid asserted) → RD_ADDR (latch addr, pre-load rdata)

RD_ADDR → (always) → RD_DATA (assert rvalid)

RD_DATA → (rvalid & rready) → IDLE

5. Implementation

Files in This Module

File	Role
tb/tb_axi_lite_standalone.v	Self-contained AXI-Lite slave + master stimulus testbench
tb/tb_axi_lite.v	Full AXI-Lite testbench with UART peripheral
tb/tb_axi_lite_master.v	Reusable AXI-Lite master task library
rtl/axi_lite_interconnect.v	Production AXI-Lite interconnect (1M → 3S)

Standalone Testbench Key Tasks (tb_axi_lite_standalone.v)

Write Task (lines 273–318):

```
task axi_write;
    input [ADDR_WIDTH-1:0] addr;
    input [DATA_WIDTH-1:0] data;
    // Phase 1: AW channel – present address, wait for awready
    // Phase 2: W channel – present data, wait for wready
    // Phase 3: B channel – wait for bvalid, de-assert bready
endtask
```

Read Task (lines 321–351):

```
task axi_read;
    input [ADDR_WIDTH-1:0] addr;
    output [DATA_WIDTH-1:0] rd_data;
    // Phase 1: AR channel – present address, wait for arready
    // Phase 2: R channel – wait for rvalid, Latch rdata
endtask
```

Slave Register Map (axi_lite_slave in standalone TB)

Address	Index	Description
0x0000	reg_file[0]	Register 0
0x0004	reg_file[1]	Register 1 (used in lab)
0x0008	reg_file[2]	Register 2
0x000C	reg_file[3]	Register 3

Address-to-index formula: $\text{index} = (\text{addr} \gg 2) \% \text{NUM_REGS}$

6. Lab / Hands-on Section

Step 1: Run the Standalone AXI-Lite Testbench

```
cd /home/coe-9/OpenLaneUser/designs/picorv32_soc/
```

Project Path: /home/coe-9/OpenLaneUser/designs/picorv32_soc/

This project is configured under the user directory coe-9.

Users accessing the project on a different account must update the username in all paths, scripts, and environment configurations accordingly.

Example:

```
/home/coe-9/ → /home/<your_username>/  
make axi_sa
```

This command: 1. Cleans obj_axi_sa/ 2. Verilates tb/tb_axi_lite_standalone.v with --binary --trace --timing 3. Runs ./obj_axi_sa/sim_axi_sa → produces tb_axi_lite_standalone.vcd 4. Opens GTKWave

Expected Terminal Output

```
=====
AXI-Lite Standalone Testbench (32-bit addr/data)
=====
```

[TB] Reset applied → All signals initialized

[TB] Starting AXI-Lite Write Transaction...

```
[WRITE] Address = 0x00000004
[WRITE] Data      = 0xa5a5a5a5
[WRITE] awvalid=1, wvalid=0 → Sending address first...
[WRITE] awready=1 → Handshake Done (address 0x00000004 accepted)
[WRITE] wvalid=1 → Sending data 0xa5a5a5a5...
[WRITE] wready=1 → Handshake Done (data accepted)
[WRITE] Waiting for bvalid...
[WRITE] bvalid=1 → Write Response Received (OKAY)
```

[TB] Starting AXI-Lite Read Transaction...

```
[READ] Address = 0x00000004
[READ] arvalid=1 → Waiting for arready...
[READ] arready=1 → Handshake Done (address 0x00000004 accepted)
[READ] Waiting for rvalid...
[READ] rvalid=1 → Data Received = 0xa5a5a5a5
```

[CHECK] Write Data == Read Data → PASS ✓

[TB] AXI-Lite Transaction Successful

```
=====
SUMMARY : Passed = 1   Failed = 0
=====
[TB] Simulation Finished
```

Step 2: View Waveforms

gtkwave tb_axi_lite_standalone.vcd &


Add signals to the wave window in order:

clk
reset
awaddr[31:0]
awvalid
awready
wdata[31:0]
wstrb[3:0]
wvalid
wready
bvalid
bready
bresp[1:0]
araddr[31:0]
arvalid
arready
rdata[31:0]
rvalid
rready
rresp[1:0]

Step 3: Run Full AXI-UART Testbench

make axi_uart

7. Waveform / Verification Insight

 

Write Transaction in GTKWave

Look for the pattern:

1. **awvalid** rises → address appears on **awaddr** → wait for **awready** to rise → **AW handshake**
2. **wvalid** rises → data appears on **wdata** → wait for **wready** to rise → **W handshake**
3. **bvalid** rises → **bready** asserted → **B handshake** (OKAY response)
4. All channels de-assert → transaction complete

Read Transaction in GTKWave

1. **arvalid** rises → address on **araddr** → **arready** rises → **AR handshake**
2. **rvalid** rises → **rdata** has the value → **rready** asserted → **R handshake**
3. Verify **rdata == wdata (0xA5A5A5A5)** → data integrity confirmed

Timing Measurement

In GTKWave, use markers to measure: - **AW handshake latency**: Cycles from **awvalid=1** to **awready=1** - **Write-to-response latency**: Cycles from **W handshake** to **B handshake** - **Read latency**: Cycles from **AR handshake** to **R handshake**

8. Common Issues & Debug Tips

Issue	Likely Cause	Fix
BVALID never asserts	AW or W handshake never completed	Check both awvalid/awready AND wvalid/wready completed
RVALID never asserts	AR handshake deadlock	Ensure arvalid held until arready seen
Data mismatch on read	Write used wrongWSTRB	VerifyWSTRB = 4'hF for full 32-bit write
Bus hangs permanently	Master de-asserted VALID before handshake	Violation of AXI rule: "never de-assert VALID before READY"
Watchdog fires (500 μ s)	Handshake deadlock	Add <code>\$display</code> inside FSM states to trace which state stuck
Multiple writes overlap	Missing B-channel completion	CPU must wait for BVALID before starting next write

AXI Protocol Violation Checklist

- ☐ AWVALID held until AWREADY seen?
- ☐ WVALID held until WREADY seen?
- ☐ BREADY asserted before or when BVALID was seen?
- ☐ ARVALID held until ARREADY seen?
- ☐ RREADY asserted before or when RVALID seen?
- ☐ No simultaneous multi-master (AXI-Lite = single master)?

9. Summary

Concept	Key Point
5 channels	AW, W, B (write side) + AR, R (read side)
Handshake rule	Transfer occurs when VALID AND READY = 1 at clock edge
WSTRB	Byte-enable mask; 4'hF = full 32-bit write
BRESP/RRESP	2'b00 = OKAY; no error in this design
Write sequence	AW handshake → W handshake → B response
Read sequence	AR handshake → R data handshake
Lab result	Write 0xA5A5A5A5 → reg[1]; Read back → 0xA5A5A5A5; PASS ✓

Previous: [Sub-module 1 — RISC-V ISA](#)

Next: [Sub-module 3 — UART Basics](#)