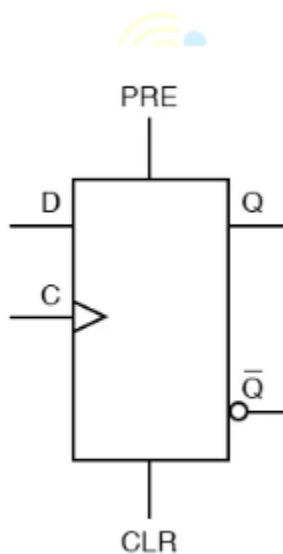


Circuit Simulation Lab:15

Design of Asynchronous Circuits

The purpose of this experiment is to introduce the design of asynchronous sequential circuits, in this case Asyn-D Flipflop. Asynchronous inputs on a flip-flop have control over the outputs (Q and not-Q) regardless of clock input status. These inputs are called the preset (PRE) and clear (CLR). The preset input drives the flip-flop to a set state while the clear input drives it to a reset state.



```
module async_dff(
input clk,
input d,
input pre,
input clr,
output reg q
);

always @(posedge clk or posedge pre or posedge clr)
begin

if(clr)
q <= 0;

else if(pre)
q <= 1;
```

```
else
    q <= d;

end

Endmodule
```

```
Testvbench
module tb_async_dff;

reg clk;
reg d;
reg pre;
reg clr;

wire q;

async_dff dut(
    .clk(clk),
    .d(d),
    .pre(pre),
    .clr(clr),
    .q(q)
);

always #10 clk = ~clk;

initial begin

    $dumpfile("async_dff.vcd");
    $dumpvars(0,tb_async_dff);

    clk = 0;
    d = 0;
    pre = 0;
    clr = 0;

    // Normal DFF Operation
    #15 d = 1;
    #20 d = 0;

    // Asynchronous Preset
```

```

#5 pre = 1;
#10 pre = 0;

// Normal Operation
#15 d = 1;

// Asynchronous Clear
#5 clr = 1;
#10 clr = 0;

// Normal Operation
#20 d = 0;
#20 d = 1;

#20;
$finish;

end

initial begin
$monitor("time=%0t clk=%b d=%b pre=%b clr=%b q=%b",
        $time,clk,d,pre,clr,q);
end

Endmodule

```



```
time=15 clk=1 d=1 pre=0 clr=0 q=0
time=20 clk=0 d=1 pre=0 clr=0 q=0
time=30 clk=1 d=1 pre=0 clr=0 q=1
time=35 clk=1 d=0 pre=0 clr=0 q=1
time=40 clk=0 d=0 pre=1 clr=0 q=1
time=50 clk=1 d=0 pre=0 clr=0 q=0
time=60 clk=0 d=0 pre=0 clr=0 q=0
time=65 clk=0 d=1 pre=0 clr=0 q=0
time=70 clk=1 d=1 pre=0 clr=1 q=0
time=80 clk=0 d=1 pre=0 clr=0 q=0
time=90 clk=1 d=1 pre=0 clr=0 q=1
time=100 clk=0 d=0 pre=0 clr=0 q=1
time=110 clk=1 d=0 pre=0 clr=0 q=0
time=120 clk=0 d=1 pre=0 clr=0 q=0
time=130 clk=1 d=1 pre=0 clr=0 q=1
time=140 clk=0 d=1 pre=0 clr=0 q=1
```